

## Experiment No. 12 Characteristics Of A Triode

### Objective:

- (a) To study the characteristics of a triode.
- (b) To study a simple amplifier circuit.

### Apparatus:

A triode mounted on a test board, power supply, a signal generator, two multimeters, a load resistor, a cathode ray oscilloscope.

### Theory:

A triode, shown schematically in Fig. 1, is a vacuum tube consisting of 3 electrodes, a cathode C, a grid G and a plate P, sealed in an evacuated envelope. The cathode C is heated by the filament F to give off electrons. The electrons are accelerated towards the plate P which is kept at a high positive potential with respect to the cathode. The grid G is a mesh of wire and it is closer to the cathode than the plate. Thus the voltage on the grid controls the flow of electrons from the cathode to the plate quite effectively.

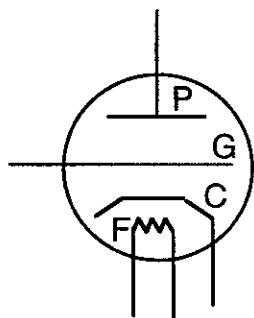


Fig. 1

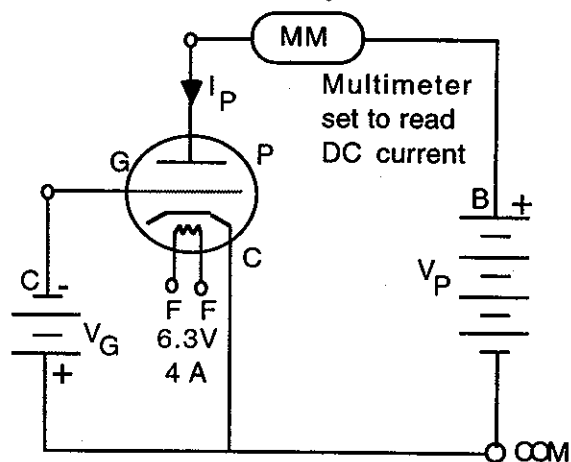


Fig. 2

Consider the triode circuit shown in Fig. 2. By keeping the grid voltage  $V_G$  constant, the plate current  $I_P$  can be measured for different values of  $V_P$ . Then a graph of  $I_P$  vs.  $V_P$  can be plotted. Three such graphs for 3 different grid voltages are shown in Fig. 3. These curves are known as the plate characteristic curves of the triode. Another type of characteristic curves of a triode are the mutual characteristic curves which are graphs of  $I_P$  vs.  $V_G$  at constant values of  $V_P$ .

Now consider the point A (Fig. 3) for which the plate current, plate voltage and grid voltage are  $I_{p2}$ ,  $V_{p1}$  and  $V_{G1}$ , respectively. If the grid voltage is reduced by  $(V_{G1} - V_{G2}) = 2$  volt, the plate current is reduced to  $I_{p1}$ . By increasing the plate voltage from  $V_{p1}$  to  $V_{p2}$ , the plate current will be restored to the value  $I_{p1}$ . The amplification factor,  $\mu$ , of a triode at a constant plate current is defined as

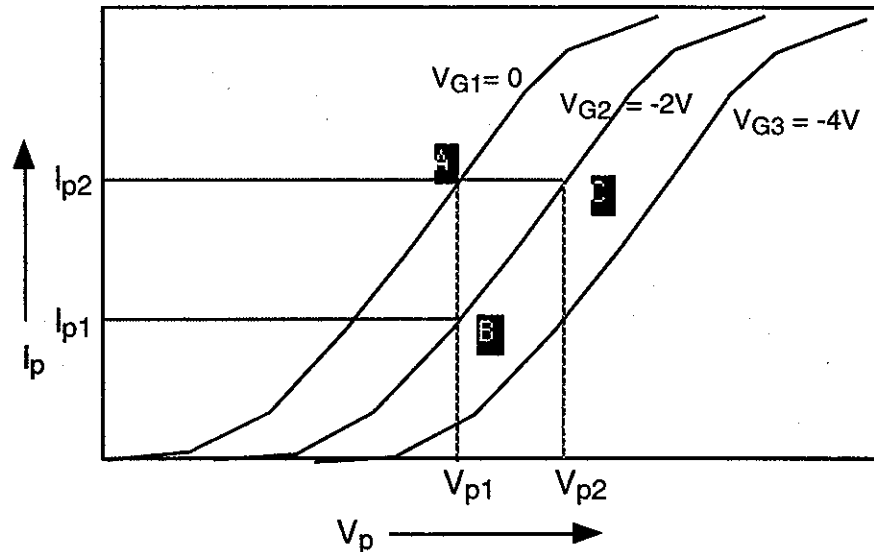


Fig. 3. Plate Characteristics Of A Triode

$$\mu = \left( \frac{V_{P2} - V_{P1}}{V_{G1} - V_{G2}} \right)_i \quad (1)$$

Another parameter of interest is the triode plate resistance  $R_p$  which is defined by

$$R_p = \frac{\Delta V_P}{\Delta I_P} \quad (2)$$

Here  $\Delta V_P$  is a small change in  $V_P$ ,  
 $\Delta I_P$  is a small change in  $I_P$ ,  
 and  $V_G$  is kept constant.

Thus if  $\Delta V_P (= V_{P2} - V_{P1})$  and  $\Delta I_P (= I_{P2} - I_{P1})$  are small (see Fig. 3),

$$R_p = \frac{V_{P2} - V_{P1}}{I_{P2} - I_{P1}} \quad (3)$$

at the grid voltage  $V_{G2}$ .

A simple amplifier circuit is shown in Fig. 4. The sine wave signal  $V_i$  from the signal generator is connected in the grid circuit. This signal is displayed on channel A of the cathode ray oscilloscope. A load resistor  $R_L$  is connected in the plate circuit and the amplified output signal obtained across  $R_L$  is displayed on channel B. The grid bias and

plate voltage are suitably adjusted to achieve amplification. If  $m$  is the amplification factor of the triode, then the input signal  $V_I$  will be amplified to  $mV_I$ . The the voltage across the total resistance ( $R_L + R_P$ ) will be  $mV_I$ , of which only the fraction

$$\frac{R_L}{R_L + R_P}$$

is obtained across load resistor  $R_L$ .

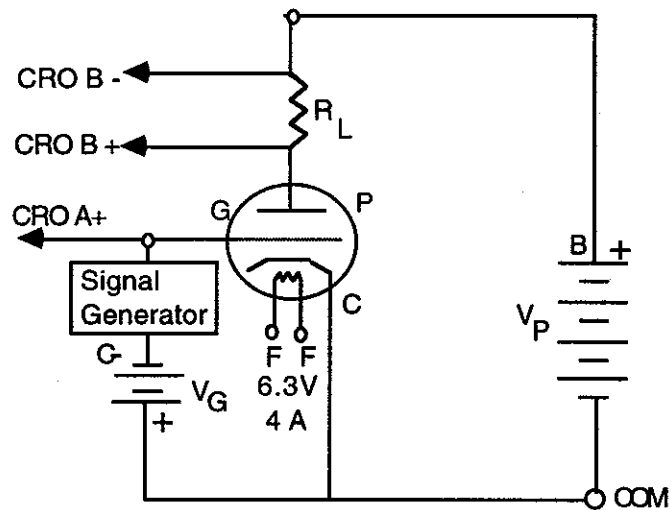


Fig. 4. A Simple Amplifier

Hence the signal  $V_A$ , across  $R_L$ , is given by

$$V_A = \frac{\mu V_I R_L}{R_L + R_P} \quad (4)$$

The amplifier gain is defined as

$$\text{gain} = \frac{\mu R_L}{R_L + R_P} \quad (5)$$

Procedure:

Unit 1: Characteristics Of A Triode:

- (a) Make the circuit as shown in Fig. 2. Connect the filament FF to its power supply (6.3V, 4A). Connect the plate to B+ of the power supply and the terminal marked com to the cathode. Connect the grid to C-. Do not include the load resistor in the circuit. Include one multimeter in the circuit to measure the plate current as shown in the figure. The second multimeter will be used to measure DC voltages as described below.

- (b) Adjust the second multimeter to read DC volts, connect it to C- and com and adjust the grid bias to -4 volt.
- (c) Now connect the second multimeter between B+ and com and adjust the plate voltage to some multiple of 10 such that the plate current (read by the first multimeter) is nearly zero. Record the plate voltage and plate current.
- (d) Increase the plate voltage in equal steps (of 10 or 15 volt) and record the plate voltage and plate current each time. Thus measure  $I_P$  for about 12 values of  $V_P$ .
- (e) Repeat the procedure by keeping  $V_G = -2$  volt and 0 volt.
- (f) Plot the plate characteristics of the triode (similar to the curves shown in Fig. 3).

#### Unit 2: Amplifier Circuit:

- (f) Measure the load resistance  $R_L$  by using the multimeter. Set up the circuit as shown in Fig. 4. Adjust the amplitude of the sine wave of the signal generator to about 2 volt and frequency to about 5000 Hz.
- (g) Switch on the oscilloscope. Set MODE to NORM, the vertical coupling (A and B) to AC. The vertical verniers should be in calibrated position. The DISPLAY can be ALT or CHOP. Set the trigger mode to AUTO (it can be changed if necessary) and adjust the trigger level if necessary. Switch on the signal generator. Set the grid bias and plate voltage corresponding to the linear segment (middle portion) of the plate characteristics. Adjust the volt/div (channels A and B) to obtain proper displays on both channels.
- (h) Record the data for Unit 2 on the data sheet.
- (i) Change  $V_I$ ,  $V_P$ ,  $V_G$ , etc. slightly to obtain more sets of data.

Note: To achieve  $V_G = 0$ , connect  $V_G$  and the grounded cathode with a black wire.



Experiment No. 12

Name:

Marks:

Partner:

Remarks:

Section:

Date Submitted:

Title:

Objective:

Theory/Formulas:

## DATA SHEET

Observations:

Unit 1: Plate Characteristic Curves:

No.	Plate voltage ( $V_p$ )	Plate Current ( $I_p$ )		
		$V_g = -4\text{ V}$	$V_g = -2\text{ V}$	$V_g = 0$
1				
2				
3				
4				
5				
6				
7				
8				
9				
10				
11				
12				

## Unit 2: Amplifier Circuit:

Load resistance  $R_L =$ 

Plate voltage =

Grid bias =

Volt/Div (A) =

Volt/Div (B) =

Peak-to-peak Height (A) =

divisions

Peak-to-peak Height (B) =

divisions

Effective value of input signal (by multimeter) =

Effective value of amplified signal (by multimeter) =

## Calculations:

Unit 1:

Plot the plate characteristics.

Use the middle portions of the curves to fill out the following.

Calculation of  $\mu$ :

Curve numbers	$V_{Gi}$	$V_{Gj}$	$V_{pi}$	$V_{pj}$	$\mu$
i=1 & j=2					
i=2 & j=3					
i=1 & j=3					



Calculation of plate resistance,  $R_p$ :

Curve number	$V_G$	$I_{pi}$	$I_{pj}$	$V_{pi}$	$V_{pj}$	$R_p$
1						
2						
3						

Unit 2:

From the above table,

$\mu =$

$R_p =$

$R_L =$

Theoretical value of gain [Eq. (5)] =

Gain (from oscilloscope readings) =

Gain (from multimeter readings) =

Questions:

1. Define the terms amplification factor, plate resistance and gain.

2. Briefly explain the working of an amplifier circuit.

3. How would you choose the operating voltages ( $V_p$  and  $V_g$ ) for the triode to function as an amplifier? What would happen if the operating voltages in Unit 2 correspond to the beginning of the plate characteristics?

4. In Unit 2, was the output signal distorted? If yes, why?